



Computer Organization and Architecture

Register Transfer and Micro- operations



ABOUT ME : MURALIKRISHNA BUKKASAMUDRAM

- MTech with 20 years of Experience in Teaching GATE and Engineering colleges
- IIT NPTEL Course topper in Theory of computation with 96 %
- IGIP Certified (Certification on International Engineering educator)
- GATE Qualified
- Trained more than 50 Thousand students across the country
- Area of Expertise : TOC,OS,COA,CN,DLD




Register Transfer and Micro-operations

RTL (Register Transfer language)

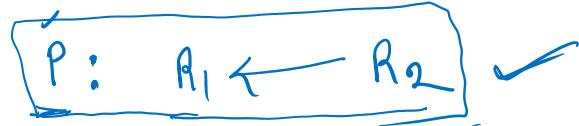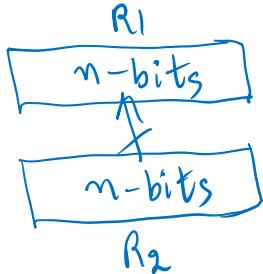


If ($P=1$) then $(R_1 \leftarrow R_2)$
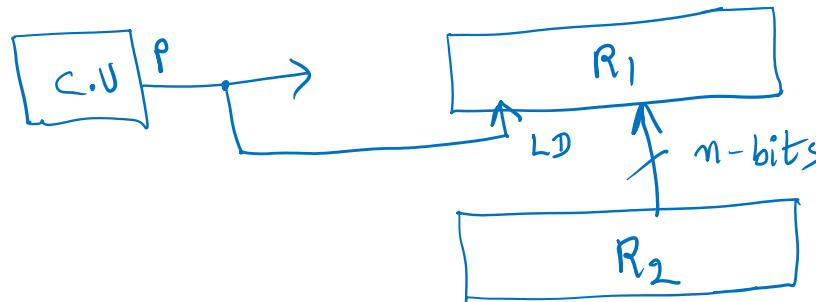
$$\begin{aligned} (\text{LD} = 1) \\ (\text{LD} = 0) \end{aligned}$$



If ($P=0$) then
 $\text{LD} = 0$

If ($P=1$) then
 $\text{LD} = 1$

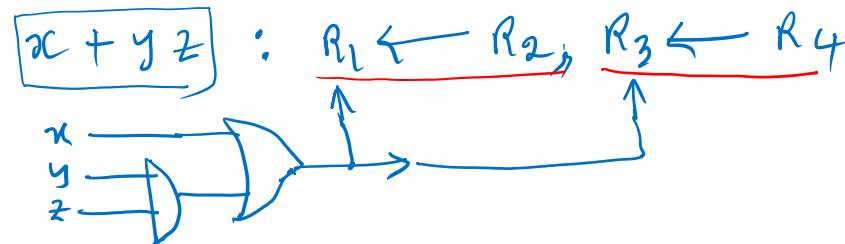

Register Transfer and Micro-operations

$$\frac{P+Q}{\uparrow} : R_1 \leftarrow R_2 + R_3 \quad \checkmark$$

$\uparrow \quad \uparrow \uparrow$

P 

$T_1 : AC(0-7) \leftarrow INPR$

If ($T_1 = 1$) then


$AC(15)$

↑

$$T_2 : OUTR \leftarrow AC(8-15)$$

: ←
 ; ()

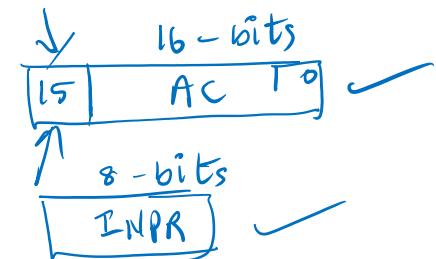Micro-Operation
 → The operation, we can perform on the data stored in the register.



$$AC(15) = 0$$

$$AC(15) = 1$$

Register Transfer and Micro-operations

Example 1 :- If ($P=1$) then ($R_1 \leftarrow R_2$) else if ($Q=1$) then ($R_3 \leftarrow R_4$)

Sol : $P : R_1 \leftarrow R_2$

$\bar{P}Q : R_3 \leftarrow R_4$


Memory Read

Read : $DR \leftarrow M[AR]$

Memory Write

Write : $M[AR] \leftarrow DR$

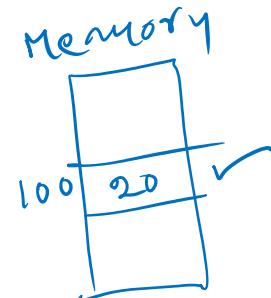
DR : Data Registers
AR : Address Registers



Register Transfer and Micro-operations

Micro - Operations

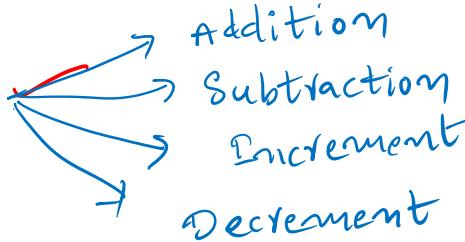- (1) Arithmetic
- (2) Logic ✓
- (3) Shift ✓



$$\begin{array}{l}
 (A + B) \\
 (A - B) \\
 (A + 1) \\
 (A - 1)
 \end{array}$$

Addition ✓

$$\begin{array}{rcl}
 A = & \overline{A_3 A_2 A_1 A_0} & HA \\
 B = & \overline{B_3 B_2 B_1 B_0} & \\
 & \overline{C_3 C_2 C_1 0} & \\
 C = & \underline{\overline{S_3 S_2 S_1 S_0}} &
 \end{array}$$

HA FA


two n-bit Registers

1 HA + (n-1) FA's.

(OR)

n - FULL Adders

Register Transfer and Micro-operations

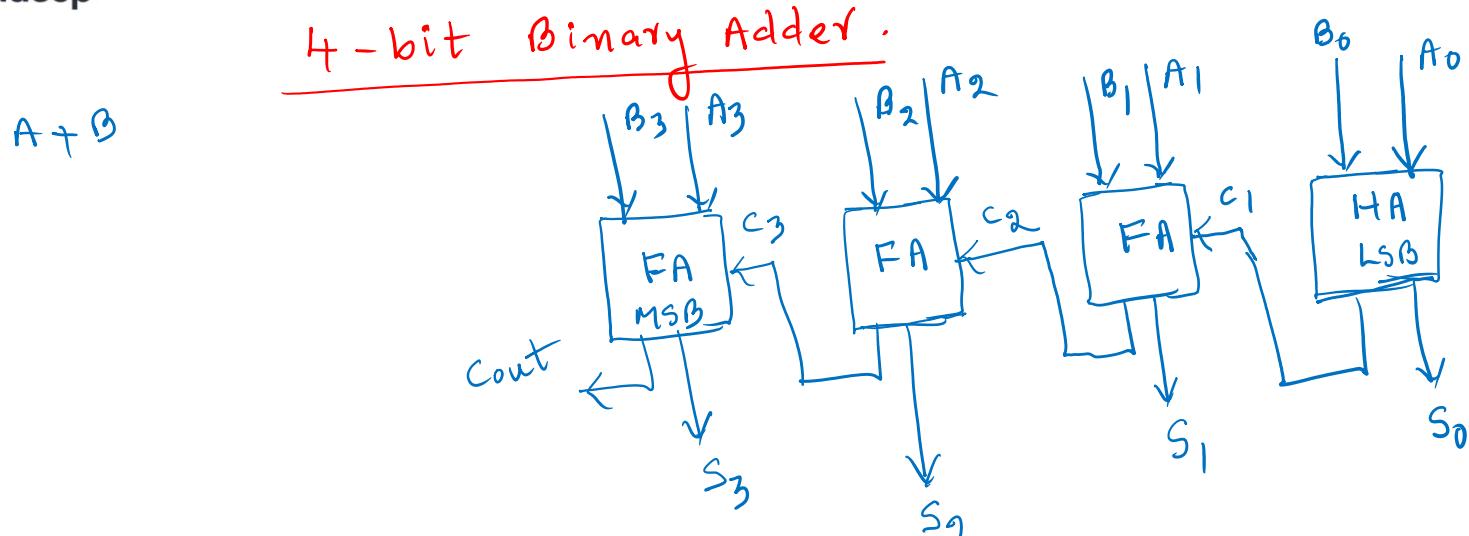
 $2(10)$

↑↑

Example :-

$$\begin{array}{r}
 A = 1001 \\
 B = 0011 \\
 \hline
 1100
 \end{array}$$

$\frac{S_3 S_2 S_1 S_0}{}$



Register Transfer and Micro-operations

$$A + B + 0 = A + B$$


$$A - B = A + (\bar{B} + 1)$$

$M = 0$ (Adder)
 $M = 1$ (Subtractor)

4-bit binary Adder Subtractor Circuit

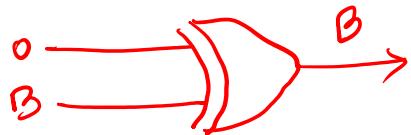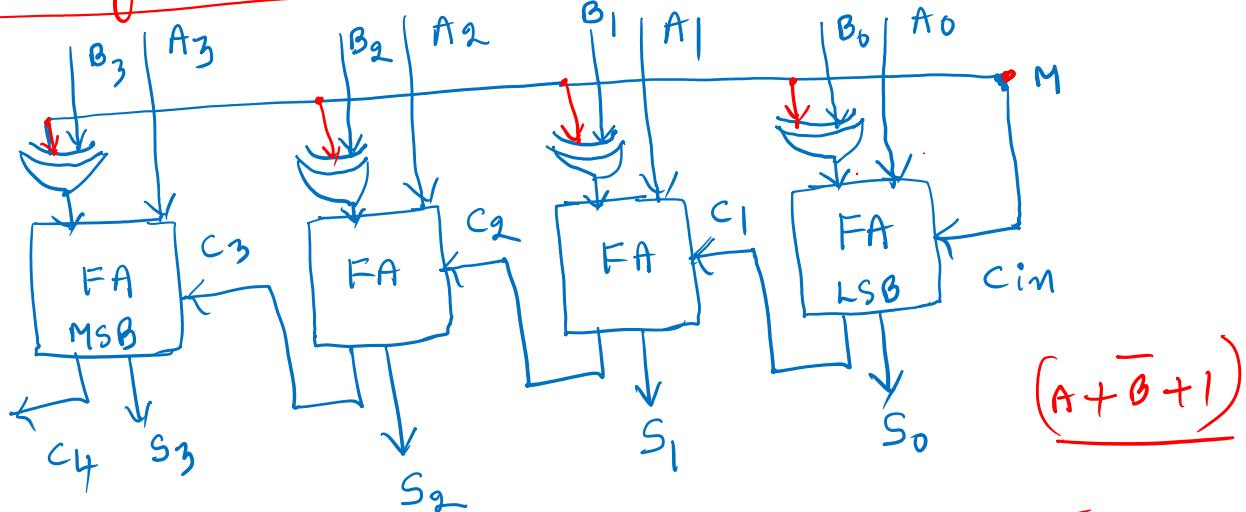


$$0 \oplus B$$

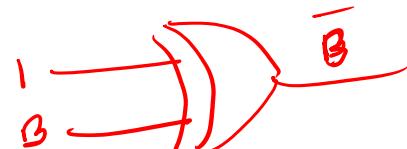

$$\begin{aligned} 0 \oplus 0 &= 0 \\ 0 \oplus 1 &= 1 \end{aligned}$$

$$\begin{aligned} 1 \oplus 0 &= 1 \\ 1 \oplus 1 &= 0 \end{aligned}$$

Register Transfer and Micro-operations

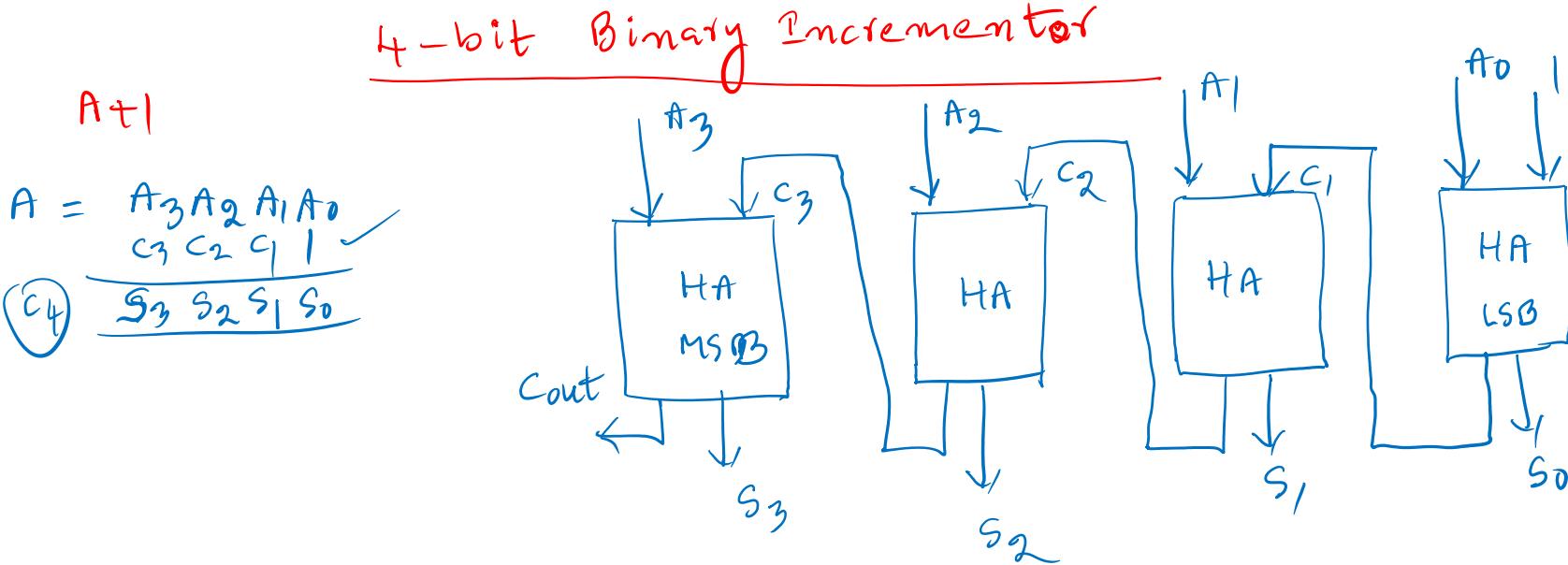

Register Transfer and Micro-operations

4-bit Binary Decrementor

$A - 1$

$A + 2^1$'s complement
of 1.

$$\begin{array}{r} 0001 \\ 1110 \\ \hline 1111 \end{array}$$

$$A = A_3 A_2 A_1 A_0$$

0 0 0 1

$$\begin{array}{r} 1110 \\ \hline 1111 \end{array}$$

1 1110


$$A = 1010$$

11110

1 1001

0000 0001

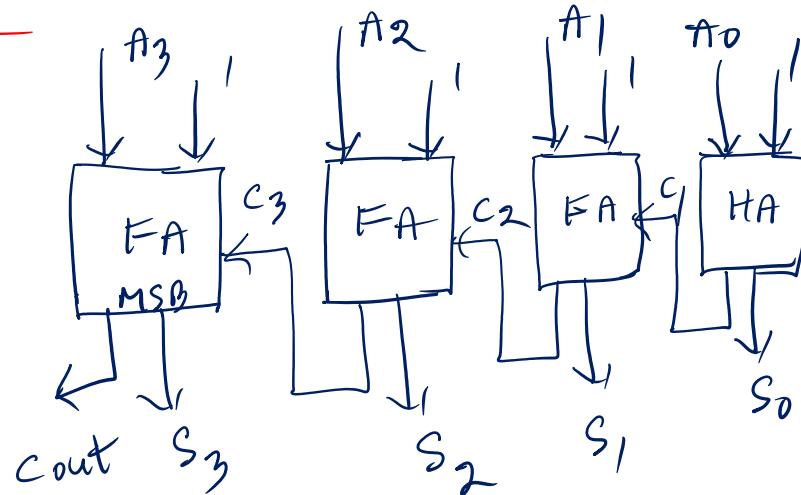
$$\begin{array}{r} 1111 1110 \\ \hline 1111 1111 \end{array}$$



Register Transfer and Micro-operations

4-bit Arithmetic Circuit

- $A + B$
- $A - B$
- $A + I$
- $A - I$

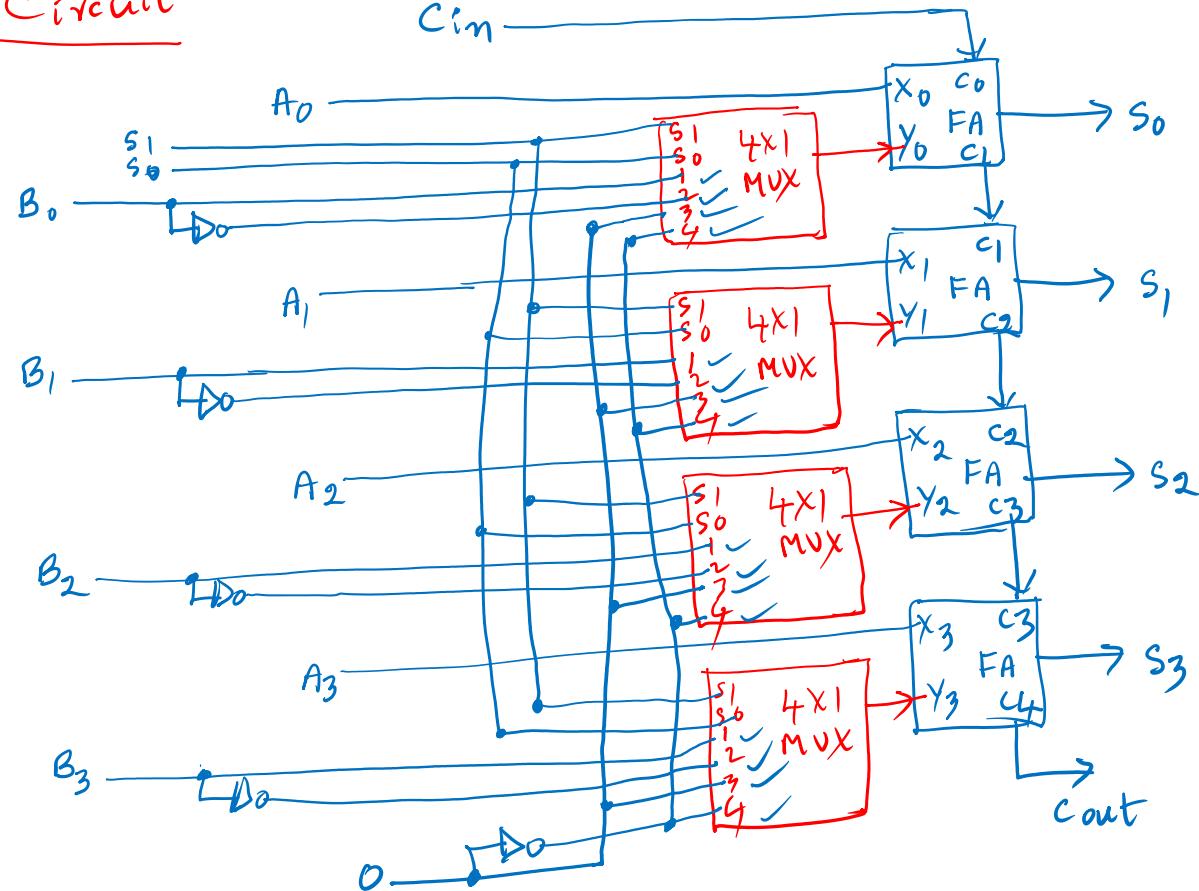

Register Transfer and Micro-operations

ADD
ADC


S_1, S_0, C_{in}	operand (Y)	$S = A + Y + C_{in}$	Micro Operation
0 0 0	B	$S = A + B$	Addition
0 0 1	B	$S = A + B + 1$	Addition with carry
0 1 0	\bar{B}	$S = A + \bar{B}$	Borrow Subtraction
0 1 1	\bar{B}	$S = A + \bar{B} + 1$	Subtraction
1 0 0	0's	$S = A$	Transfer
1 0 1	0's	$S = A + 1$	Increment
1 1 0	1's	$S = A - 1$	Decrement
1 1 1	1's	$S = A - 1 + A$	Transfer

Register Transfer and Micro-operations


Shift Micro-Operations

- (1) Logical Shift $\xrightarrow{\text{lshl}}$ $\xrightarrow{\text{lshr}}$
- (2) Circular Shift $\xrightarrow{\text{cil}}$ $\xrightarrow{\text{cir}}$
- (3) Arithmetic Shift $\xrightarrow{\text{ashl}}$ $\xrightarrow{\text{ashr}}$

Logical shift Left

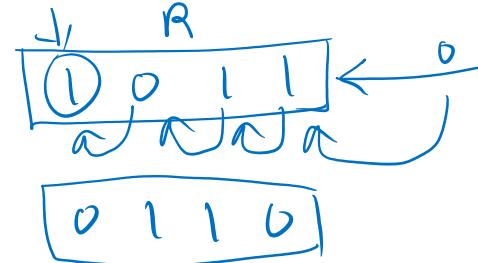


Logical shift Right

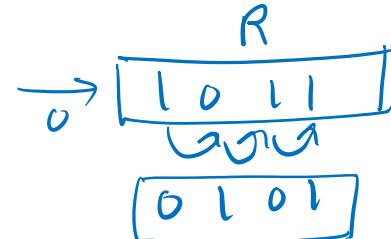


Register Transfer and Micro-operations

Circular Shift Left

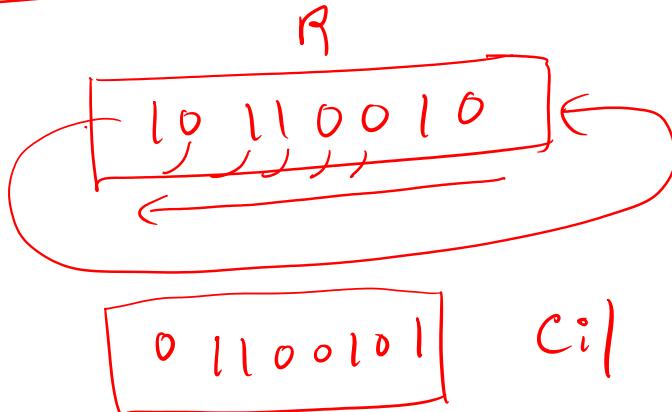

Circular Shift Right

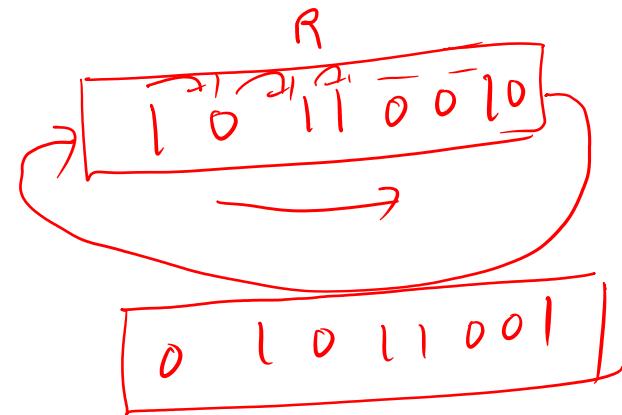


Register Transfer and Micro-operations

Arithmetic Shift Left (ashl)

$$+5 \times 2 = +10$$
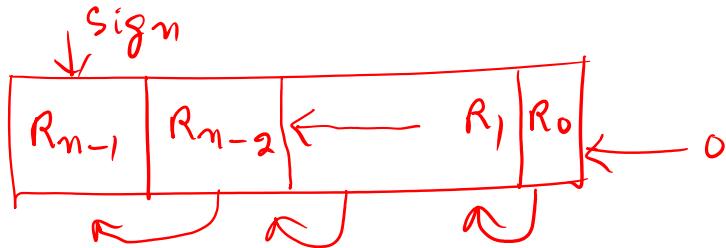
$$\begin{array}{r} 0101 \\ \oplus \\ 0101 \end{array} \quad 0 \oplus 0 = 0$$



$$V_s = R_{n-1} \oplus R_{n-2}$$

$$+10 \times 2 = +20$$

$$\begin{array}{r} 01010 \\ \oplus \\ 10100 \end{array} \quad 0 \oplus 1 = 1$$

this multiply
the given signed
integer by 2.

Register Transfer and Micro-operations

Divides the given signed integer by 2

Arithmetic Shift Right (ashr)

